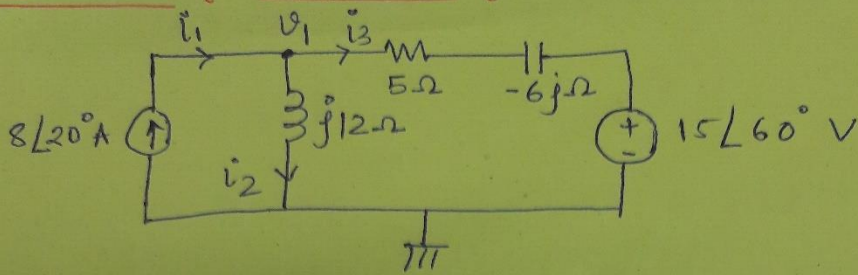


Nodal analysis for AC circuits:- (Example)



find the node voltage V_1 & branch currents i_1, i_2, i_3

Solution:- Using KCL at node V_1 .

$$\vec{i}_1 = \vec{i}_2 + \vec{i}_3$$

$$8\angle 20^\circ = \frac{V_1}{j12} + \frac{V_1 - 15\angle 60^\circ}{(5 + (-6j))}$$

$$8\angle 20^\circ = V_1 \left[\frac{1}{j12} + \frac{1}{5-6j} \right] - \frac{15\angle 60^\circ}{7.81\angle -50.194^\circ}$$

$$\rightarrow 7.517 + j2.736 = V_1(-0.0833j + 0.0819 + 0.093j) - 1.9206\angle 110.194^\circ$$

$$7.517 + j2.736 = V_1[0.0819 + 0.0147j] + 0.663 - 1.8025j$$

$$V_1 = \frac{7.517 - 0.663 + j2.736 + 1.8025j}{(0.0819 + 0.0147j)}$$

$$V_1 = \frac{6.854 + 4.5385j}{0.0819 + 0.0147j} = \frac{90.711 + 39.133j}{0.0819 + 0.0147j}$$


$$= 98.792\angle 23.33^\circ \text{ V}$$

$$i_2 = \frac{v_1}{j12} = 3.260 + (-7.559)j = \underline{8.23 \angle -66.67^\circ \text{ A}}$$

$$i_3 = \frac{v_1 - 15 \angle 60^\circ}{5 - 6j}$$

$$v_3 = 4.28 + 10.327j = \underline{11.167 \angle 67.629^\circ \text{ A}}$$

Find the node voltages V_1 and V_2 .

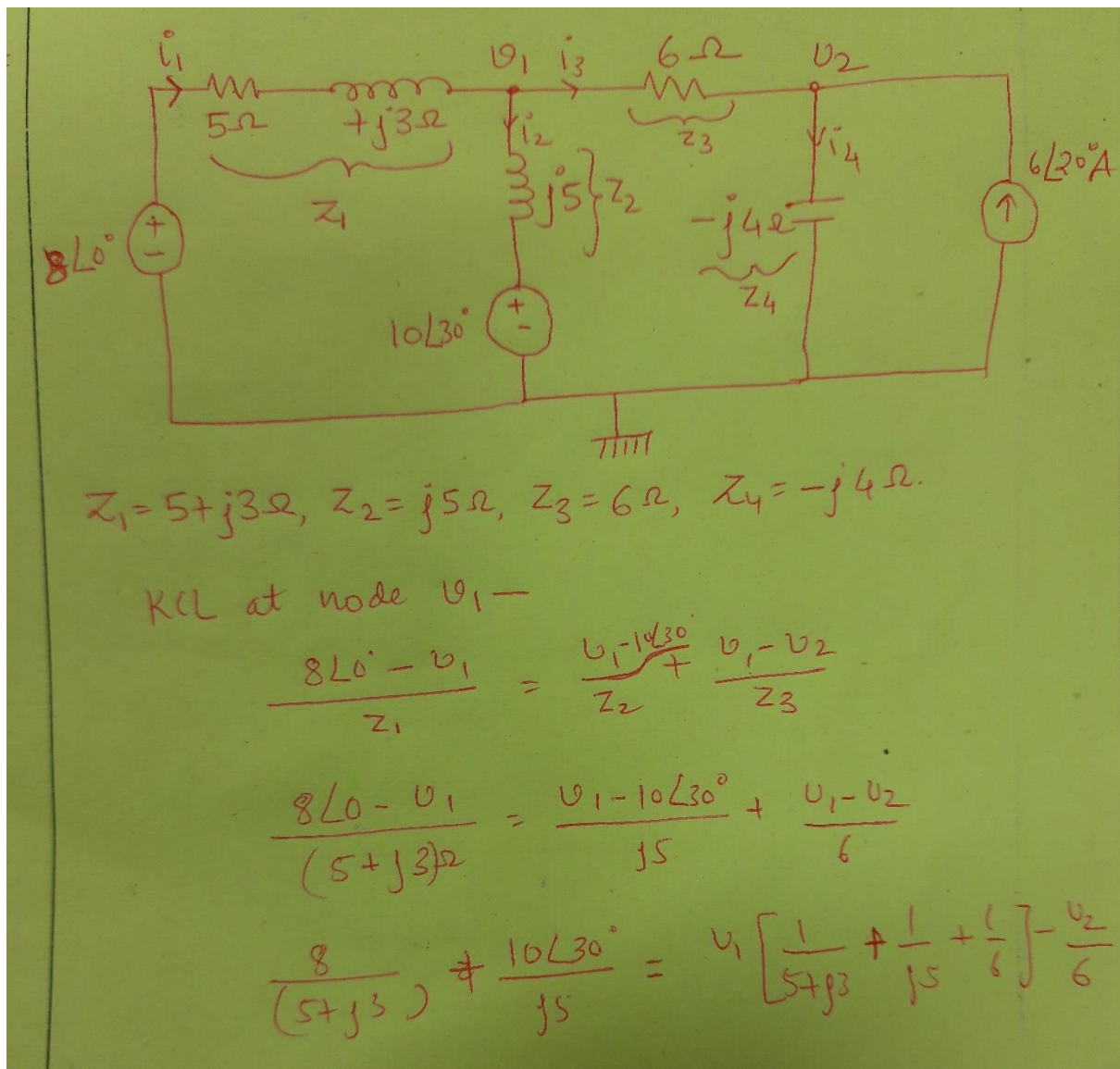

$$1.1764 + (-0.705)j + 1 - 1.732j = V_1(0.5137 - 0.088j) - \frac{V_2}{6}$$

$$2.1764 - 2.437j = V_1(0.5137 - 0.088j) - \frac{V_2}{6} \quad \text{--- (1)}$$

KCL at node V_2 -

$$\overline{I_3} + 6\angle 20^\circ = \overline{I_4}$$

$$\frac{V_1 - V_2}{6} + 6\angle 20^\circ = \frac{V_2}{-j4}$$

$$\frac{V_1}{6} - V_2 \left[\frac{1}{6} - \frac{1}{j4} \right] = -6\angle 20^\circ$$


$$\frac{V_1}{6} - V_2(0.166 + 0.25j) = -5.638 - 2.052j \quad \text{--- (2)}$$

$$\begin{bmatrix} 0.5137 - 0.088j & -1/6 \\ 1/6 & -(0.166 + 0.25j) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 2.1764 - 2.437j \\ -5.638 - 2.052j \end{bmatrix}$$

Solve using cramer rule - for V_1 & V_2 .

→ Exercise.

* Mesh analysis for AC circuit (example)

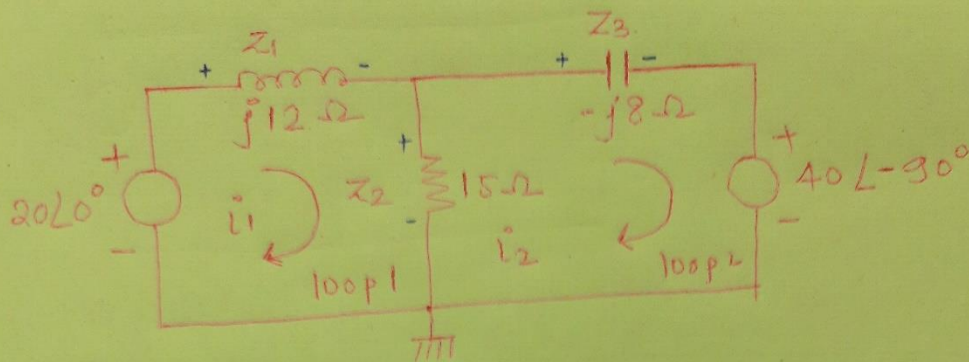

For loop 1, using KVL-

$$20\angle 0^\circ - I_1 Z_1 - (I_1 - I_2) \cdot Z_2 = 0$$

$$20\angle 0^\circ - I_1 (j12) - (I_1 - I_2) \cdot 15 = 0$$

$$j12 I_1 + 15 I_1 - 15 I_2 = 20\angle 0^\circ$$

$$I_1 (15 + j12) - 15 I_2 = 20\angle 0^\circ$$

$$19.209\angle 38.659^\circ I_1 - 15 I_2 = 20\angle 0^\circ \quad \text{--- (1)}$$

for loop 2, using KVL-

$$15(I_1 - I_2) - Z_3 I_2 - 40\angle -90^\circ = 0$$

$$15 I_1 - 15 I_2 - (-j8) I_2 = 40\angle -90^\circ$$

$$15 I_1 - (15 - j8) I_2 = 40\angle -90^\circ$$

$$15 I_1 - 17\angle -28.07^\circ I_2 = 40\angle -90^\circ \quad \text{--- (2)}$$

$$\begin{bmatrix} 15+j12 & -15 \\ 15 & -15+j8 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 20 \angle 0^\circ \\ 40 \angle 90^\circ \end{bmatrix}$$

$$\begin{bmatrix} 15+j12 & -15 \\ 15 & -15+j8 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 20 \\ -40j \end{bmatrix}$$

using Crammer's rule -

$$\Delta = -36 - 60j = 113.207 \angle -147.99^\circ$$

$$\Delta_1 = \begin{bmatrix} 20 & -15 \\ -40j & -15+j8 \end{bmatrix} = -300 - 440j = 532.54 \angle -124.3^\circ$$


$$I_1 = \frac{\Delta_1}{\Delta} = 4.307 + 1.891j = 4.704 \angle 23.703^\circ \text{ A}$$

$$\text{similarly, } \Delta_2 = \begin{bmatrix} 15+j12 & 20 \\ 15 & -40j \end{bmatrix} = \frac{180 - 60j}{626.41 \angle -73.3^\circ} \text{ A}$$


$$I_2 = \frac{\Delta_2}{\Delta} = \frac{189.74 \angle -18.43^\circ}{113.207 \angle -147.99^\circ} = 1.676 \angle 129.55^\circ \text{ A}$$

$$I_2 = \Delta_2 / \Delta = \frac{626.41 \angle -73.3^\circ}{113.207 \angle -147.99^\circ} = 5.53 \angle 74.68^\circ \text{ A}$$

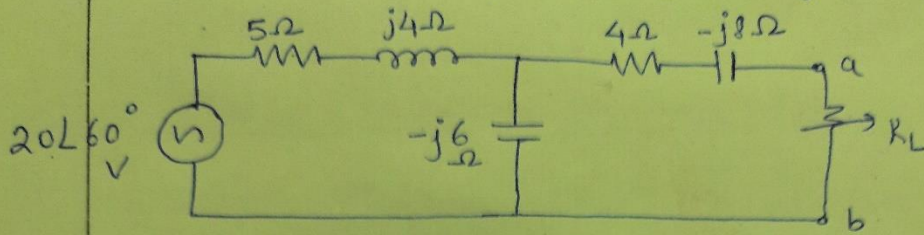Find the Thevenin's equivalent for the following ckt



for V_{th} -

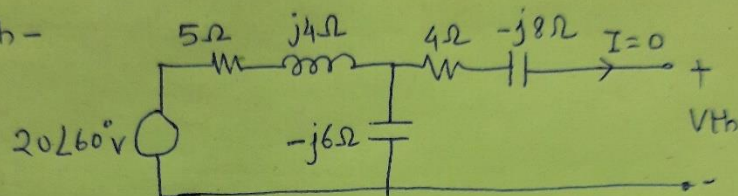


V_{th} = voltage across $-j6\Omega$.

using voltage division principle

$$V_{-j6\Omega} = V_{th} = \frac{20\angle 60^\circ \times (-j6\Omega)}{5\Omega + j4\Omega - j6\Omega}$$

$$V_{th} = 22.055 + (-3.177j) = \underline{\underline{22.283\angle -8.198^\circ V}}$$


for Z_{th} -

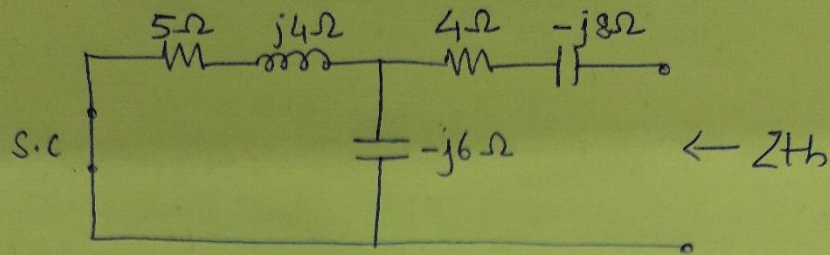

$$Z_{th} = (5 + j4)\Omega \parallel (-j6\Omega) + (4 - j8)\Omega$$


$$= 6.2068 - 3.517j + 4\Omega - j8\Omega$$
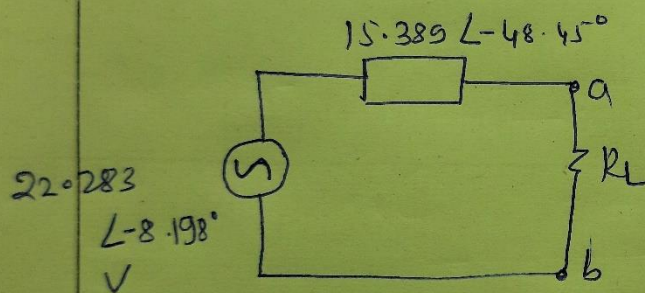
$$= 10.2068 - 11.517j = 15.389 \angle -48.45^\circ$$



Superposition Theorem for AC Network:-

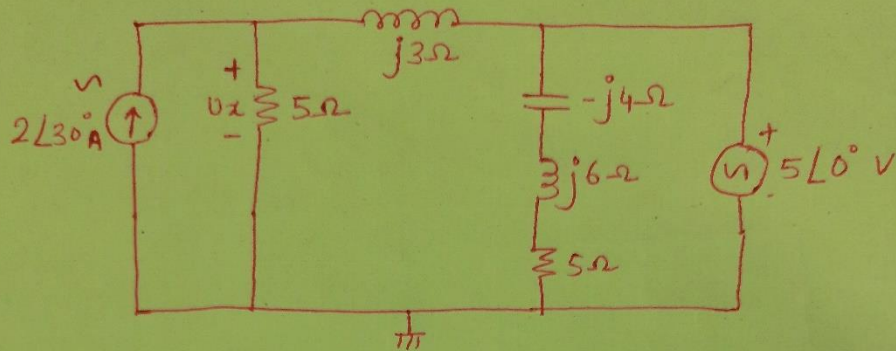For the following network find voltage ' V_x ' using superposition theorem.




using current source alone. Modified ckt will be -

→ using current division principle -

$$I_{5\Omega}' = \frac{2\angle 30^\circ \times j3\Omega}{5 + j3\Omega}$$

$$= 0.0173 + j1.0288 \text{ A}$$
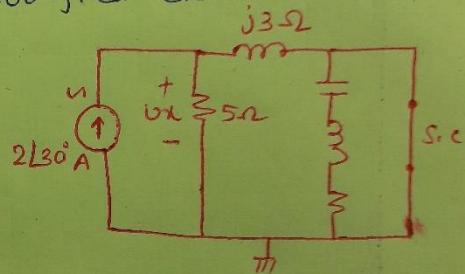
$$= 1.0289 \angle 89.03^\circ \text{ A}$$




$$\therefore V_x' = 5 \times I_{5\Omega}'$$

$$= 5.1445 \angle 89.03^\circ \text{ V}$$

Considering voltage source alone. The modified ckt will be using voltage division principle.

$$V_x'' = \frac{5 \times 5\angle 0^\circ}{5 + j3} = 3.676 + j2.205 \text{ V}$$
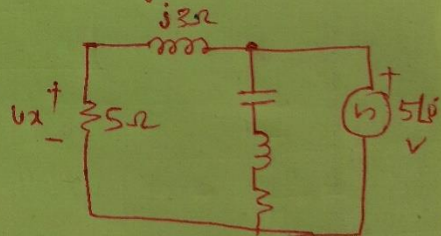
$$V_x'' = 4.287 \angle -30.963^\circ \text{ V}$$



$$V_x = V_x' + V_x'' = 5.1445 \angle 89.03^\circ + 4.287 \angle -30.963^\circ$$

$$= 3.763 + j2.9381 = 4.774 \angle 37.90^\circ \text{ V}$$