

Examples :-

- ① A generator is coupled to a steam turbine. Calculate the speed of the turbine if the alternating frequency (rotational) of the generated sinusoid is 50Hz.

→ Assume that the generator is a two pole generator.

→ Solution :-

Little background :-

* For one complete cycle of voltage waveform, the coil/conductor move past one pair of N & S poles.

∴ P = total no. of poles = $2p$ (p - no. of pairs of pole).

f = frequency of generated voltage Hz.

N = speed of rotor (or, turbine) in rev/min.

$$f = \frac{\text{No. of cycles}}{\text{seconds}} = \frac{\text{No. of cycles}}{\text{revolutions}} \times \frac{\text{revolutions}}{\text{seconds}}$$

$$= \frac{P}{2} \times \frac{N}{60}$$

$$\boxed{f = \frac{PN}{60 \times 2}}$$

∴ speed of ^{steam} turbine = $N = \frac{120f}{P} = \frac{120 \times 50}{2}$

~~generator~~

$$\boxed{N = 3000 \text{ rev/min}}$$

- ② A hydro-turbine ~~is~~ speed ~~is~~ maintained at 150 rev/min. Find the no. of poles to generate 50Hz sinusoidal output voltage.

Solution :-

$$N = \frac{120f}{P}, \quad P = \frac{120f}{N}$$

$$P = \frac{120 \times 50}{150} = 40 \text{ poles.}$$

(or, 20 pole pairs)

- ③ In an AC excited circuit, $v(t) = 200 \sin(100t - 20^\circ) \text{ V}$
 & $i(t) = 20 \sin(100t + 40^\circ) \text{ A}$
 find R, Z & X .

Solution :- $V_m = 200 \text{ V}, I_m = 20 \text{ A}.$

$$\bar{V} = \frac{200 \text{ V}}{\sqrt{2}} \angle -20^\circ, \quad \bar{I} = \frac{20 \text{ A}}{\sqrt{2}} \angle 40^\circ$$

$$\bar{Z} = \frac{\bar{V}}{\bar{I}} = \frac{200 \angle -20^\circ}{20 \angle 40^\circ} = 10 \angle -20^\circ - 40^\circ = 10 \angle -60^\circ \Omega$$

explanation - $\bar{Z} = \frac{200 \angle -20^\circ}{20 \angle 40^\circ} = \frac{200 \cdot e^{-j20}}{20 \cdot e^{j40}}$

$$\bar{Z} = 10 \cdot e^{-j(20-40)} = 10 e^{-j60}$$

$$\bar{Z} = 10 \angle -60^\circ \Omega = 10(\cos 60^\circ - j \sin 60^\circ)$$

$$\bar{Z} = 5 - 8.66j \Omega = R - jX_C$$


$$\therefore \boxed{R = 5 \Omega}, \boxed{X_C = 8.66 \Omega}$$

$$|Z| = \sqrt{5^2 + 8.66^2} = 10 \Omega$$

capacitor value can be found from -


$$X_C = \frac{1}{\omega C}; \quad C = \frac{1}{X_C \omega} = \frac{1}{8.66 \times 2 \times 100}$$

$$\boxed{C = 1.15 \text{ mF}}$$

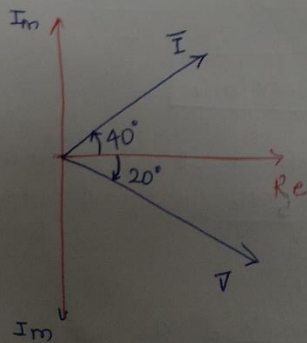

(* - ~~the~~ Phasor diagram is drawn for illustration. It is not needed to solve the problem).

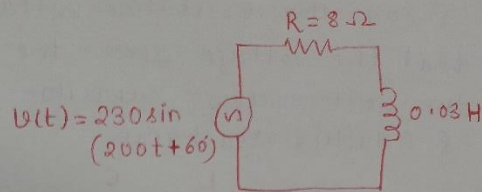④ For the given series R-L circuit, find the current.



Solution :- $X_L = j\omega L = j \times 200 \times 0.03 = 6j \Omega$.

$$Z = R + j\omega L = 8 + 6j \Omega = \sqrt{8^2 + 6^2} \angle \tan^{-1}\left(\frac{6}{8}\right)$$


$$Z = 10 \angle 36.87^\circ \Omega$$

$$\begin{aligned} \bar{i}(t) &= \frac{v(t)}{Z} \quad \text{or} \quad \bar{I} = \frac{\bar{V}}{\bar{Z}} \\ &= \frac{230}{10 \angle 36.87^\circ} = \frac{230 \angle 60^\circ}{10 \angle 36.87^\circ} \end{aligned}$$


$$\bar{I} = 23 \angle 60 - 36.87 = 23.13^\circ$$

$$\therefore \bar{I} = 23 \angle 23.13^\circ \text{ A.}$$
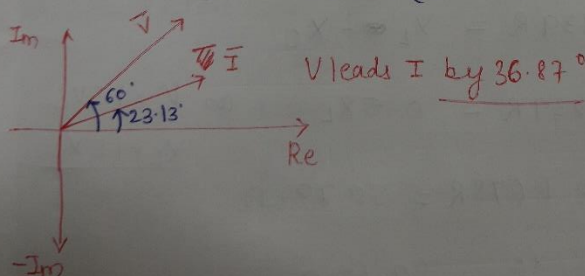
$$i(t) = 23.8 \sin(200t + 23.13^\circ) \text{ A.}$$



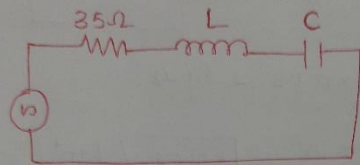- ⑤ For the following ckt, $R = 35 \Omega$. The circuit current i lags the excitation voltage by 40° . Assuming that the voltage across the ^{inductor}~~capacitor~~ is 1.5 times the voltage across capacitor. find the capacitive & inductive reactance.



Solution :-

using phasor diagram approach -

$$V_L = 1.5 V_C \rightarrow (\text{given}).$$

$\hookrightarrow \therefore$ ckt is inductive in nature

$$\therefore \phi = \tan^{-1} \left(\frac{V_L - V_C}{V_R} \right)$$

$$40^\circ = \tan^{-1} \left[\frac{X_L - X_C}{R} \right]$$

$$0.839 R = X_L - X_C$$

$$0.839 R = 0.5 X_L \quad \text{as } V_L = 1.5 V_C$$

$$X_L = 1.678 R = 58.73 \Omega$$

$$X_C = \frac{X_L}{1.5} = 39.15 \Omega$$

Capacitive Reactance = 39.15Ω , Inductive Reactance = 58.73Ω

Note, Since the excitation frequency is not mentioned, the value of L & C can not be determined.

- ⑥ In the following series R-C circuit, $R = 100\Omega$, $C = 100\mu F$
Find - (i) current, i (ii) Phase shift between V & I
(iii) V_C (iv) V_R (v) Power consumed.

Solution :-

$$\text{Impedance } Z = R - \frac{j}{\omega C}$$

$$Z = 100\Omega - \frac{j}{2\pi \times 50 \times 100 \times 10^{-6}}$$

$$Z = 100\Omega - 31.83j\Omega = 104.94\Omega \angle -17.656^\circ$$

$$(i) \bar{I} = \frac{\bar{V}}{\bar{Z}} = \frac{230 \angle 0^\circ}{104.94 \angle -17.656^\circ} = 2.192 A \angle +17.656^\circ$$

(ii) current leads voltage by 17.656° .

Instantaneous expression of voltage & current -

$$v(t) = 230\sqrt{2} \sin \omega t V. \quad (230V - \text{RMS value})$$

$$i(t) = 2.192 \times \sqrt{2} \sin(\omega t + 17.656^\circ) A.$$

Voltage across Cap.


$$(iii) V_C = I \times X_C$$

$$= 2.192 \times 31.83 = \underline{69.77V.}$$

$$(iv) V_R = I \times R = 2.192 \times 100 = 219.2V.$$


$$(v) \text{Power consumed} = \text{Power dissipated in } R = I^2 R$$
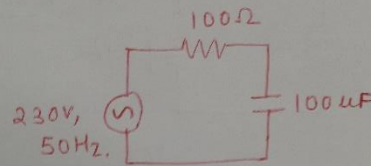
$$= 100 \times 2.192^2 = \underline{\underline{480.48W}}$$



$$\omega = 2\pi f = 2\pi \times 50 \\ = 100\pi = 314 \text{ rad/s}$$

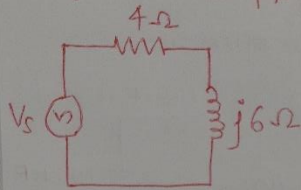- ⑦ For the below given R-L circuit, $I = 4A$ (RMS value).
find the supply voltage.



* Solution :-

$$Z = 4 + j6 \Omega$$

$$|Z| = \sqrt{4^2 + 6^2} = 7.21 \Omega$$

$$\phi = \tan^{-1}\left(\frac{6}{4}\right) = 56.31^\circ$$

$$\bar{V} = \bar{Z} \bar{I}$$

$$= 7.21 \angle 56.31^\circ \times 4A \angle 0^\circ$$

$$\bar{V} = 28.84 \angle 56.31^\circ$$

if, $i(t) = 4\sqrt{2} \sin \omega t A$ then -

$$\rightarrow v(t) = 28.84\sqrt{2} \times \sin(\omega t + 56.31^\circ)$$

Voltage leads current
by 56.31° .


- e). ⑤ An AC voltage $= (80 + 60j) \text{ V}$ is applied to a circuit. The current flowing through the circuit is $(-4 + 10j) \text{ A}$. Find impedance, power consumed & phase angle.

* Solution :-

$$V = 80 + 60j = 100 \angle 36.86^\circ \text{ V}$$

$$I = -4 + 10j = 10.77 \angle -68.198^\circ \text{ A}$$

using phasor diagram-

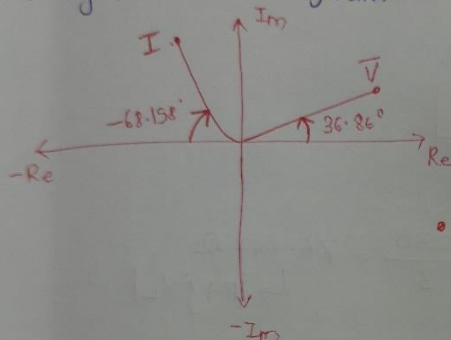

Net phase shift betⁿ I & V

$$\phi = 180^\circ - [36.86^\circ + 68.198^\circ]$$

$$\phi = 74.942^\circ$$

• Current leads voltage by 74.942°

$$\text{power factor} = \cos \phi = 0.2597 \text{ (leading)}.$$

$$\text{power consumed} = VI \cos \phi$$

$$= 100 \times 10.77 \times \cos \phi$$

$$= 279.69 \approx \underline{280 \text{ W}}$$

Alternate way to compute power consumed.

$$\text{Power consumed} = \text{Re} \{ \bar{V} I^* \}, \quad \begin{aligned} I &= -4 + 10j \\ I^* &= -4 - 10j \end{aligned}$$

$$\text{Power consumed} = \text{Re} \{ (80 + 60j) \times (-4 - 10j) \}$$

$$= \text{Re} \{ 320 - 800j - 240j + 600 \} = \text{Re} \{ \underline{280} - 1040j \}$$

$$\therefore \text{Power consumed} = \underline{280 \text{ W}}$$

[Note - -1040 is the reactive power]

- ⑨ ^{Immersion (coil)}
A heater consumes 3A of current when powered from a 230V, 50 Hz AC. The heater consumes 300W of power. Calculate resistance, impedance & inductance of the heater.

Note :-

Solution :-

$$\text{Power consumed} = I^2 R$$

$$300 = 3^2 \times R$$

$$R = 33.33 \Omega$$

$$V = I \times Z$$

$$\therefore Z = \frac{V}{I} = \frac{230}{3} = 76.667 \Omega$$

$\hookrightarrow |R + jX_L|$

$$Z^2 = R^2 + X_L^2$$

$$76.66^2 = 33.33^2 + X_L^2$$

$$X_L = \sqrt{76.66^2 - 33.33^2}$$

$$X_L = 69.035 \Omega$$

$$\therefore Z = 33.33 + j69.035 \Omega$$

$$X_L = \omega L = 69.035$$

$$\therefore L = \frac{69.035}{2\pi \times 50} = \underline{\underline{0.219 \text{ H}}}$$


- ⑩ A coil of resistance 15Ω & inductance 60mH , a pure non-inductive resistor of 30Ω & loss-free $30\mu\text{F}$ capacitor are connected in series across 230V , 50Hz supply. Calculate: (a) Current

- (b) Voltage across capacitor & the coil
(c) Power consumed in circuit
(d) Power consumed by coil
(e) Power factor of the circuit.

* Solution :- Total Resistance = Res. of coil + Resistor
 $= 15 + 30 = 45\Omega$.

$$X_L = 2\pi fL = 2\pi \times 50 \times 60 \times 10^{-3}$$

$$X_L = 18.85\Omega$$

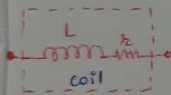

$$X_C = \frac{1}{2\pi fC} = \frac{106.10\Omega}{}$$

$$\text{Coil impedance} = |Z_C| = \sqrt{R^2 + X_L^2} = \sqrt{15^2 + 18.85^2}$$

$$|Z_C| = 24.09\Omega$$

$$\text{Net impedance of ckt } Z_T = R + j(X_L - X_C)$$

$$|Z_T| = \sqrt{R^2 + (X_L - X_C)^2} = 98.17\Omega$$

a) Current, $I = \frac{V}{|Z_T|} = \frac{230}{98.17} = 2.342\text{A (rms)}$.

b) Voltage across cap = $I \times X_C = 248.48\text{V}$,
 Voltage across coil = $I \times X_L = 44.1467\text{V}$.

c) Power consumed in ckt = $I^2 \times R_T = \frac{10539\text{W}}{I^2 \times 45} = 246.82\text{W}$

d) Power consumed in coil = $I^2 \times R = 82.27\text{W}$.

e) Power factor, $\cos \phi = \frac{R}{Z_T} = \frac{45}{98.17} = 0.458$

* Since, $X_C > X_L$
 pf is leading