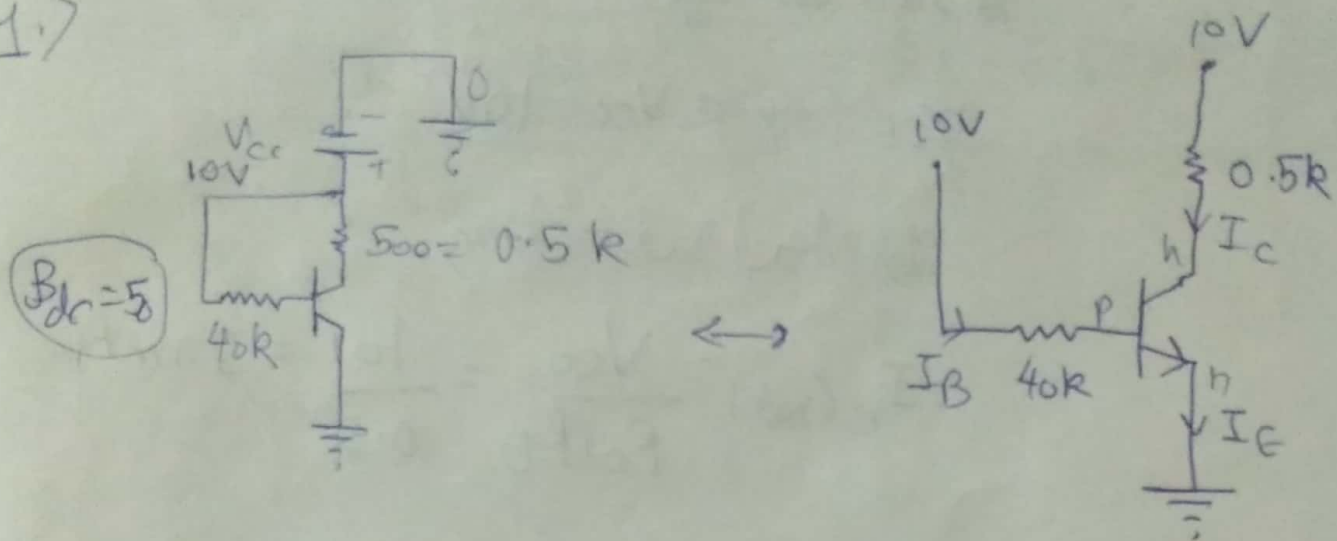


Assignment on BJT

1.7



i/p KVL -

$$10 - 40I_B - 0.7 = 0$$

$$\Rightarrow I_B = \frac{9.3}{40} \text{ mA} = 0.2325 \text{ mA}$$

$$I_C = \beta I_B = 50 \times 0.2325 = \cancel{6.975 \text{ mA}} = 11.625 \text{ mA}$$

$$I_E = I_B + I_C = \cancel{7.2075 \text{ mA}} = 11.8575 \text{ mA}$$

o/p loop KVL -


$$10 - 0.5 \times 11.625 - V_{CE} = 0$$

$$\therefore V_{CB} = V_{CE} - V_{BE} = 3.48 \text{ V} > 0$$

$$\boxed{V_{CE} = \cancel{6.5125 \text{ V}}} \quad \boxed{V_{CB} = 4.1875 \text{ V}}$$

Q-point is $(\cancel{6.5125 \text{ V}}, \cancel{6.975 \text{ mA}})$

$(4.1875 \text{ V}, 6.975 \text{ mA})$

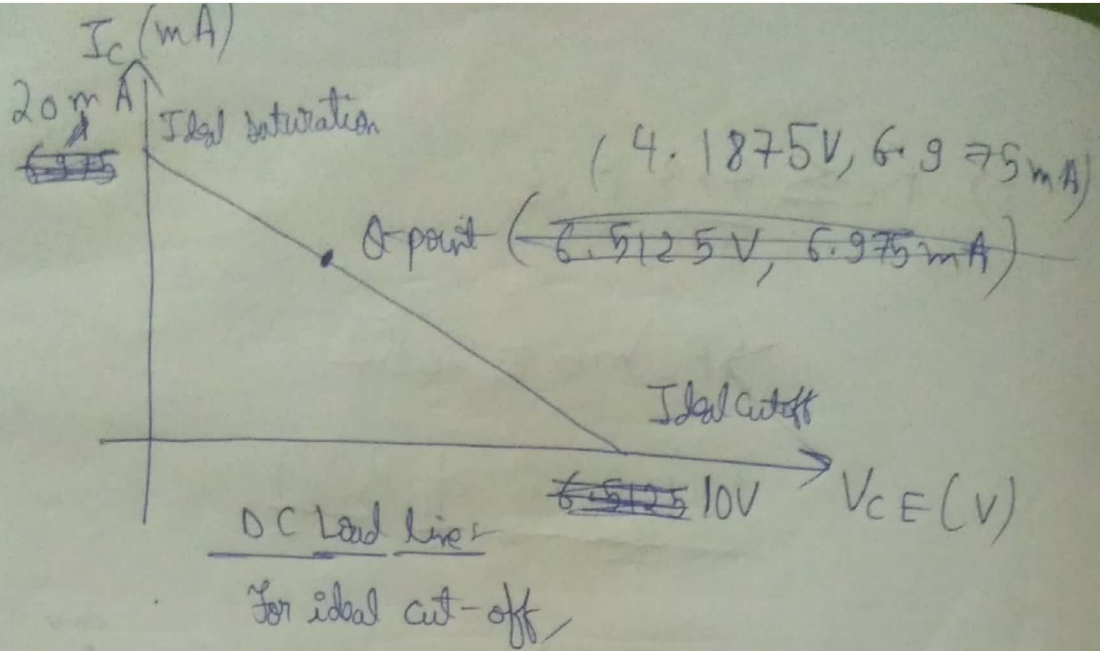


For ideal cut-off,

$$V_{CE}(\text{off}) = V_{CC} = 10 \text{ V}$$

For ideal saturation,

$$I_C(\text{sat}) = \frac{V_{CC}}{R_C + R_E} = \frac{10}{0.5} = 20 \text{ mA}$$

2.)

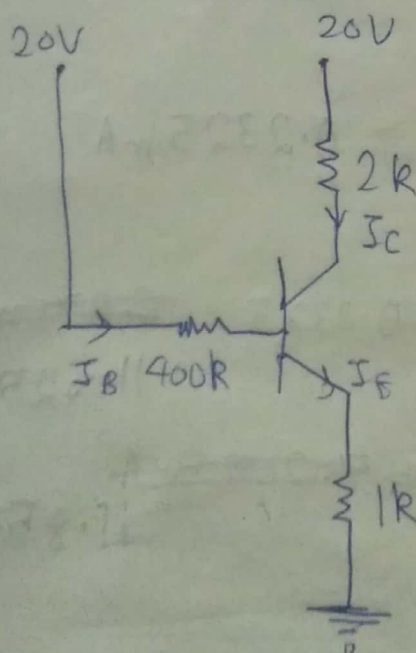

solⁿ: Given, $\beta_{DC} = 50$

and $I_C \neq I_E$

i/p loop KVL-

$$20 - 400I_B - 0.7 - (\beta + 1)I_B = 0$$

$$\Rightarrow 19.3 = 45I_B$$

$$\Rightarrow \boxed{I_B = 0.0428 \text{ mA}}$$

o/p loop KVL-

$$20 - 2 \times 50 \times 0.0428 - V_{CE} - 51 \times 0.0428 = 0$$

$$\Rightarrow \boxed{V_{CE} = 13.5372 \text{ V}}$$

$$\therefore V_{CE} = V_{CE} - V_{BE} \\ = 12.8372 \text{ V} > 0$$


$\therefore$ Active Region

$$I_C = 50 \times I_B = 2.14 \text{ mA}$$


For cutoff, $V_{CE}(\text{off}) = V_{CC} = 20 \text{ V}$

For satⁿ
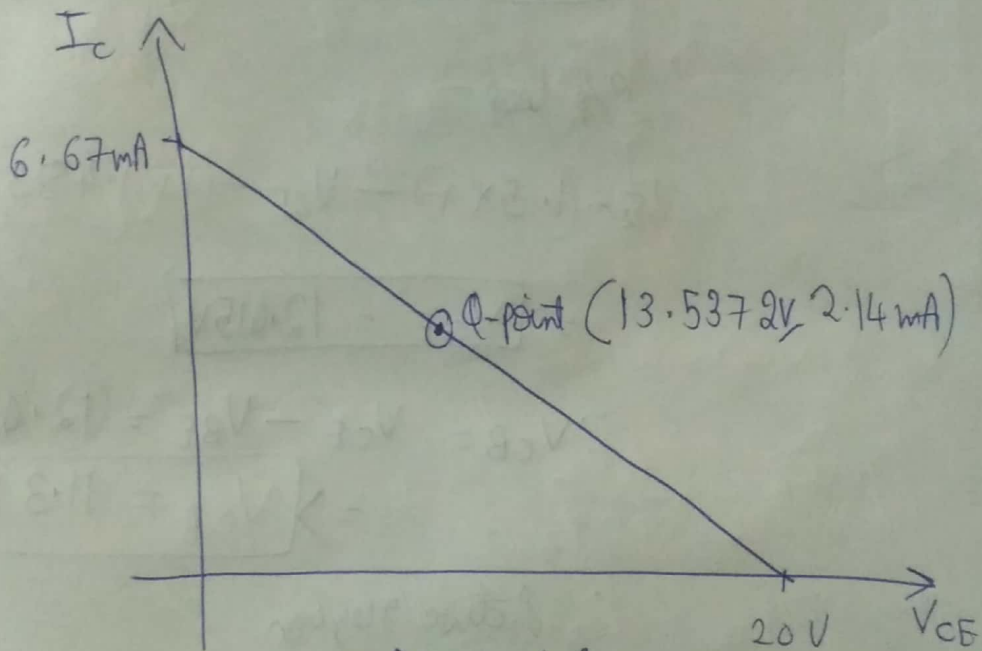
$$I_C(\text{sat}) = \frac{V_{CC}}{2+1} = \frac{20}{3} = 6.67 \text{ mA}$$



DC Load line

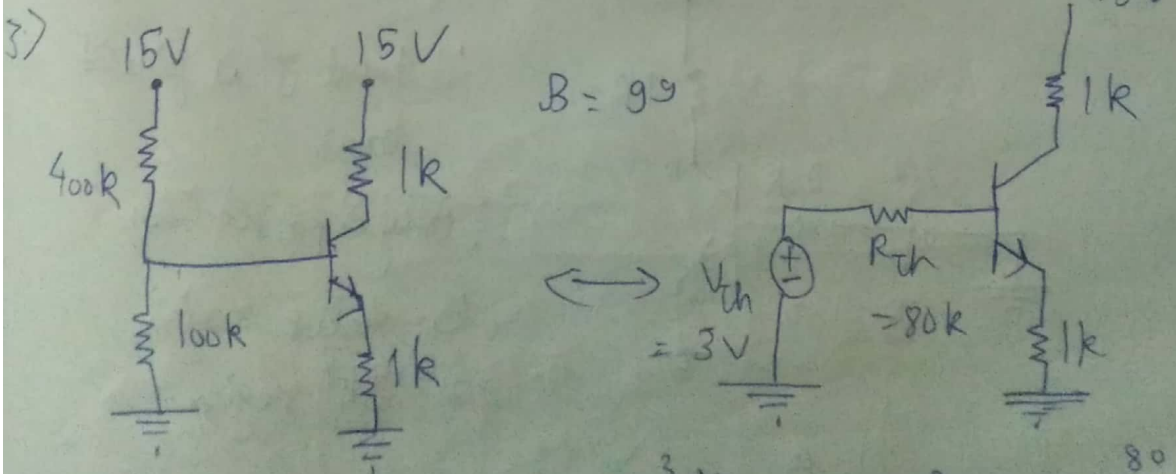

$$V_{th} = \frac{15}{5} \times 1 = 3 \text{ V}, R_{th} = \frac{100 \times 400}{500} = 80 \text{ k}$$

i/p loop —

$$3 - 80I_B - 0.7 - 100I_B = 0$$

$$\Rightarrow I_B = \frac{2.7}{180}$$

$$\Rightarrow I_B = 0.015 \text{ mA}$$

$$I_C = 1.485 \text{ mA}$$

$$I_E = 1.500 \text{ mA}$$

o/p loop —

$$15 - (1.5 \times 1) - V_{CE} - (1 \times 1.485) = 0$$


$$\Rightarrow V_{CE} = 12.015 \text{ V}$$

$$\therefore V_{CB} = V_{CE} - V_{BE} = (12.015 - 0.7) \text{ V}$$

$$\Rightarrow V_{CB} = 11.315 \text{ V}$$

$\therefore$ Active region

4. >

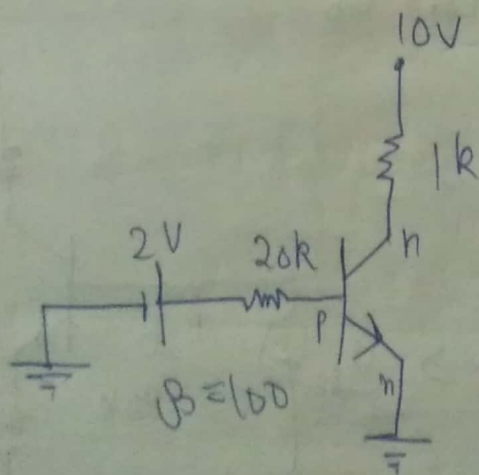

$\therefore$ Input J^n is forward bias

$\therefore$ Only 2 possibilities

① Active region

② Satⁿ region.

Let us assume active region

i/v loop.

$$2V - 20 \times I_B - 0.7 = 0$$

$$\Rightarrow I_B = 0.065 \text{ mA}$$

$$I_C = 100 \times I_B = 6.5 \text{ mA}$$

By KCL,

$$I_E = 6.565 \text{ mA}$$

O/p loop -

$$10 - 1 \times 6.5 - V_{CE} = 0$$

$$\Rightarrow V_{CE} = 3.5 \text{ V}$$

$$\text{Now, } V_{CB} = V_{CE} - V_{BE}$$


$$= (3.5 - 0.7) \text{ V}$$

$$= 2.8 \text{ V}$$

$$\therefore V_{CB} > 0 \text{ V}$$

Clearly, O/p J^n is reverse bias

$\therefore$ our assumption is correct.

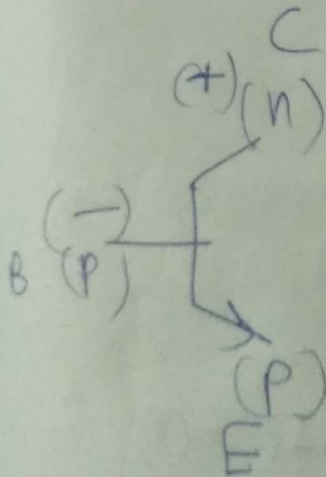

Hence, Active region.

5.)


Given,

$$I_C = 1 \text{ mA}$$

$$\beta_{dc} = \infty \Rightarrow$$

$$I_B = 0 \Rightarrow I_C = I_E$$

$$V_{BE} = 0.7 \text{ V}$$

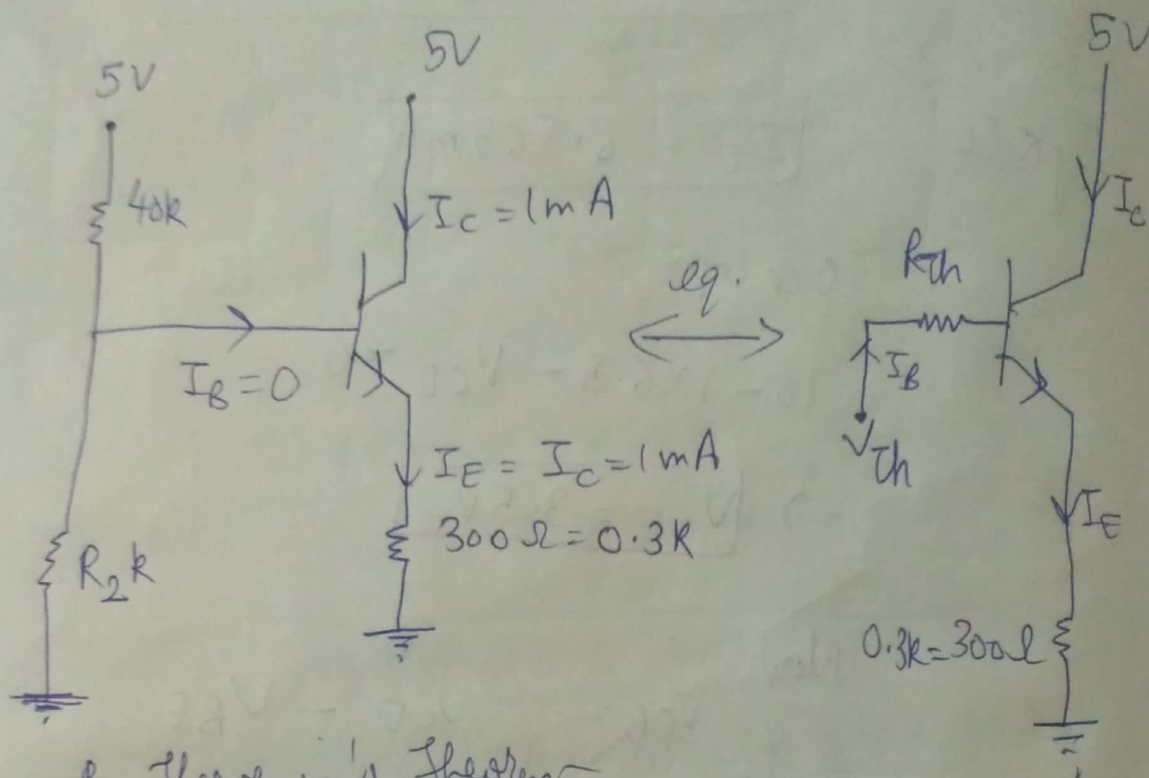

By Thevenin's Theorem

$$V_{Th} = \frac{5 R_2}{40 + R_2}$$

$$R_{Th} = \frac{40 R_2}{40 + R_2}$$

$\therefore$ i/p KVL-

$$V_{Th} - 0 \times R_{Th} - 0.7 - 0.3 \times I_E = 0$$

$$\Rightarrow V_{Th} = 0.3 \times 1 + 0.7$$

$$\Rightarrow \frac{5 R_2}{40 + R_2} = 1 \Rightarrow 4 R_2 = 40$$


$$\Rightarrow R_2 = 10 \text{ k}\Omega$$

6.7

For DC analysis, $\omega = 0$


$$\Rightarrow X_C = \frac{1}{\omega C} = \infty$$

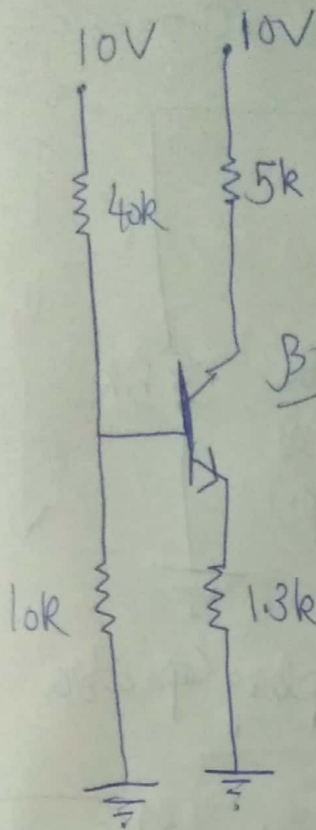$\therefore$ All Capacitors are open-circuited



$\beta = \infty$

eq.
 $\longleftrightarrow$

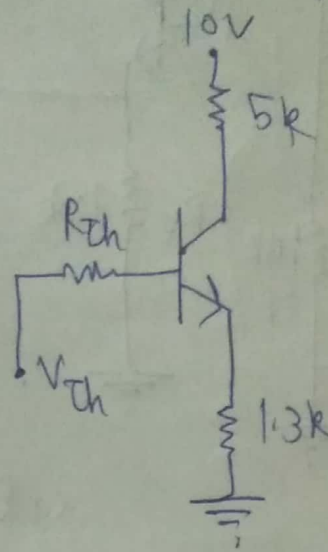

By Thevenin's Theorem —

$$V_{Th} = \frac{10 \times 10}{50} = 2V$$

$$R_{Th} = \frac{10 \times 40}{10 + 40} = 8k\Omega$$

i/p loop KVL —


$$V_{Th} - 0 \times R_{Th} - 0.7 - (I_C \times 1.3) = 0$$

$$\left[\because \beta = \infty \Rightarrow I_B = 0 \right. \\ \left. \Rightarrow I_E = I_C \right]$$

$$I_C = \frac{2 - 0.7}{1.3} \Rightarrow I_C = 1mA$$

$$\Rightarrow I_E = 1mA$$

77

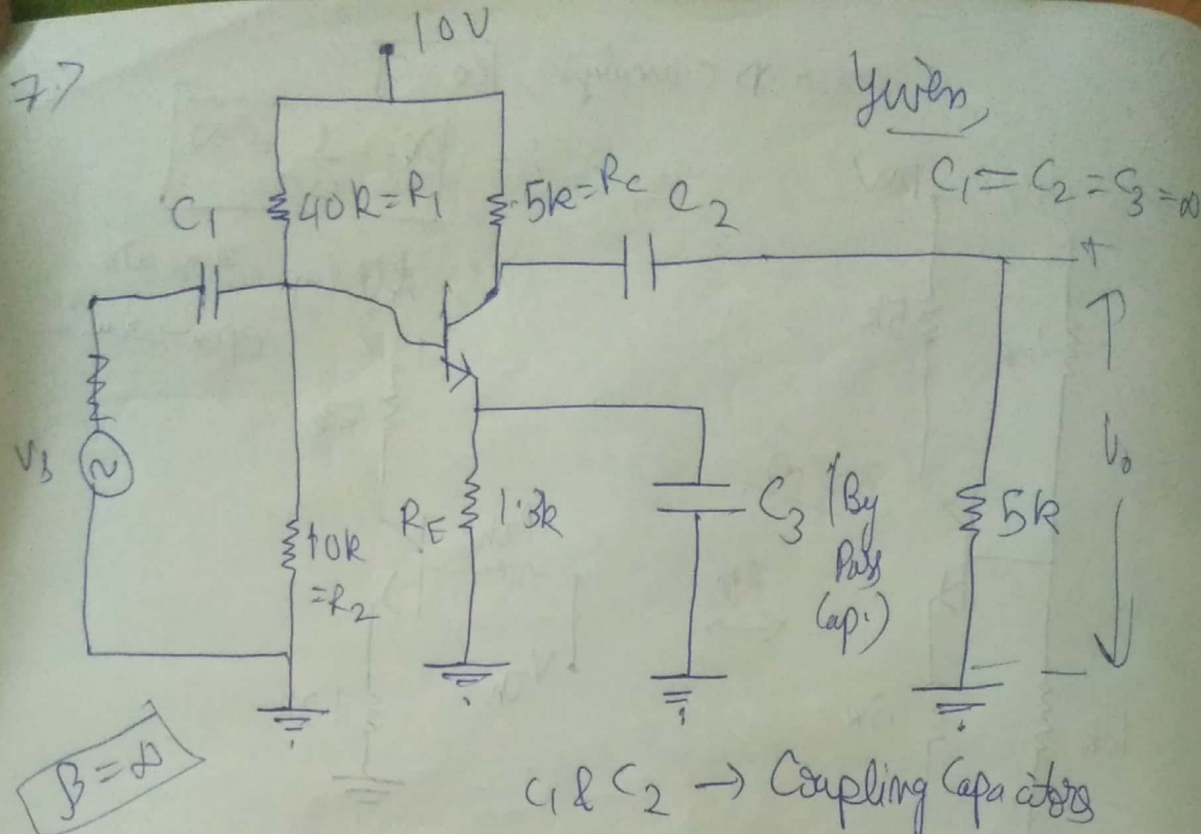

For AC signal, $\omega \neq 0$

$$X_C = \frac{1}{\omega C} = \frac{1}{\infty} \Rightarrow X_C = 0$$


$\therefore$ Capacitors are short-circuited

The given circuit is fixed-bias
(for good thermal stability)


We use bypass capacitor to increase gain

as gain $\downarrow$ when $R_E \uparrow$ (All current pass through C_3)

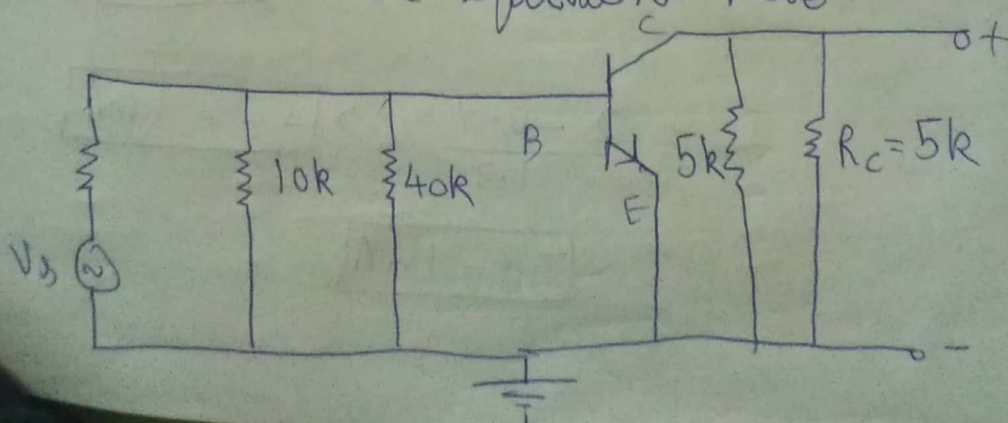Step I:- Short circuit all dc sources and emitter resistance, as well as all capacitors for ac equivalent model


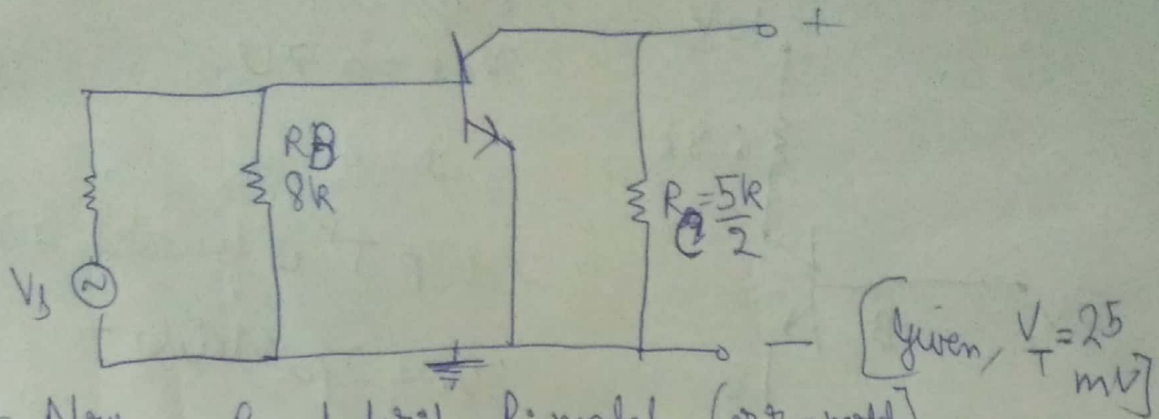
$$R_{eq} = \frac{10 \times 40}{10 + 40} = \frac{400}{50} \Rightarrow R_{eq} = 8k$$




Now, By hybrid- π model (or π model)

$$i_c = g_m V_{BE} = i_E \quad (\because \beta = \infty)$$

$V_{BE} \approx V_T$
(for small signal)

$$\Rightarrow \frac{V_{BE}}{i_E} = \frac{1}{g_m} \Rightarrow g_m = \frac{1}{25 \text{ mV}} = 40 \text{ A/V}$$
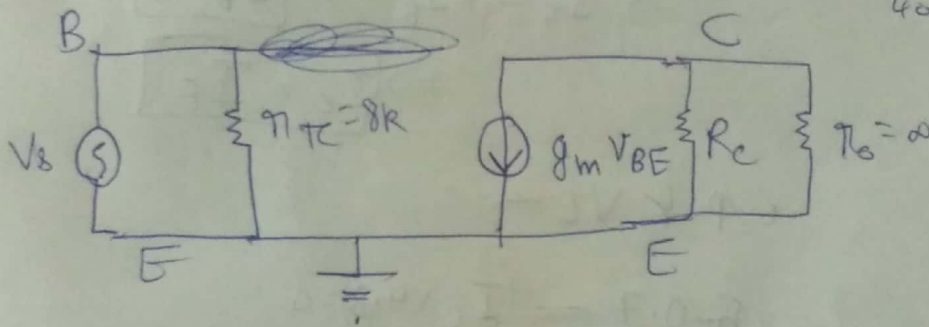
$$\Rightarrow r_e = \frac{1}{40} \Omega$$




$$Z_i = R_B \parallel (\beta + 1) r_e = R_B = 8k$$

$$Z_o = r_o \parallel R_C = \frac{5}{2} \parallel \infty = \frac{5}{2} k$$

$$A_v = \frac{V_o}{V_i} = \frac{-\beta i_b R_C}{i_b (\beta + 1) r_e} = -\frac{R_C}{r_{\pi}} \quad (\because \beta \approx (\beta + 1))$$

$$= -\frac{5}{2 \times 8}$$

$$\Rightarrow A_v = -\frac{5}{16}$$

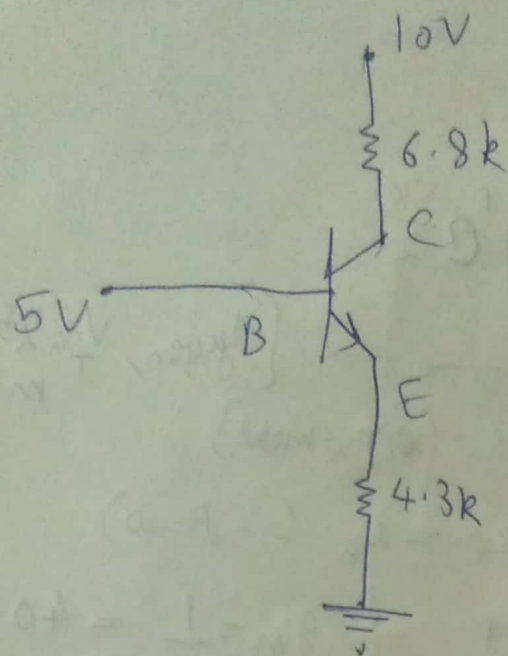

Given,

$$V_{BE} = 0.7V$$

$$\beta = \infty$$

$\therefore$ i/p J^n is forward biased

$\therefore$ Only 2 possibilities -

① Satⁿ region

② Active region

Assume ② active region -

$$\Rightarrow I_C = \beta I_B \Rightarrow \boxed{I_B = 0}$$

$$\Rightarrow \boxed{I_C = I_E}$$

i/p KVL -

$$5 - 0.7 - (I_C \times 4.3) = 0$$

$$\Rightarrow I_C = \frac{4.3}{4.3}$$

$$\Rightarrow \boxed{I_C = 1mA}$$

o/p KVL -

$$10 - (6.8 \times 1) - V_{CE} - (4.3 \times 1) = 0$$

$$\Rightarrow \boxed{V_{CE} = -1.1V}$$

$$V_{CB} = V_{CE} - V_{BE} = -1.1 - 0.7$$

$$\Rightarrow \boxed{V_{CB} = -1.8V} \Rightarrow V_{CB} < 0$$

$\therefore$ as assumption is wrong $\therefore$ o/p J^n is forward bias
 $\therefore$ (Satⁿ region)

9.)

When C & B of a transistor are shorted,
it acts as a p-n junction diode

Given,

$$I_S = 10^{-14} \text{ A}$$

$$\eta = 1$$

$$V_{BE} = 0.7 \text{ V}$$

$$I = I_S \left(e^{\frac{V_{BE}}{\eta V_T}} - 1 \right)$$

At room temperature,

$$V_T = \frac{T}{11600} = \frac{300}{11600} = 0.026 \text{ V}$$

$$\therefore I = 10^{-14} \left(e^{(0.7)/0.026} - 1 \right)$$


$$= 4.9266 \times 10^{-3} \text{ A}$$

$$\boxed{I = 4.9266 \text{ mA}}$$

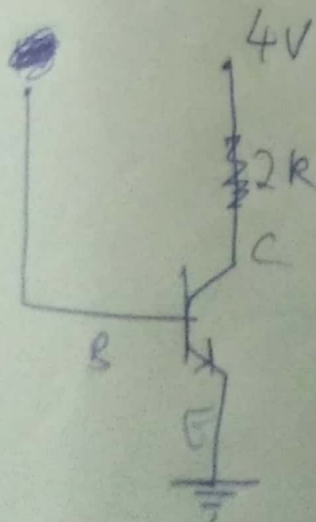10.)

Given,

$$V_{CE}(\text{sat}) = 0.2 \text{ V}, \beta_{dc} = 200$$



By KVL -

$$4 - 2I_C - V_{CE}(\text{sat}) = 0$$

$$\Rightarrow \frac{3.8}{2} = I_C$$

$$\Rightarrow \boxed{I_C = 1.9 \text{ mA}}$$

$$\Rightarrow (I_B)_{\min} = \frac{I_C}{\beta} = \frac{1.9 \text{ mA}}{200}$$

$$\Rightarrow \boxed{(I_B)_{\min} = 9.5 \mu\text{A}}$$