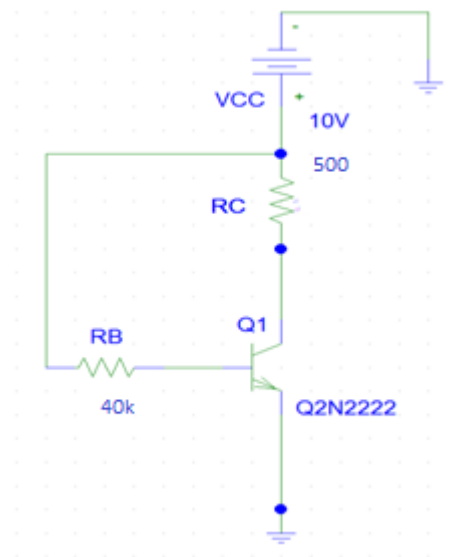



Questions on BJT, 2019

Dhananjay De


1. Draw the dc load line of the given circuit and calculate the Q-point values of I_C and V_{CE} . Consider $\beta_{dc} = 50$.



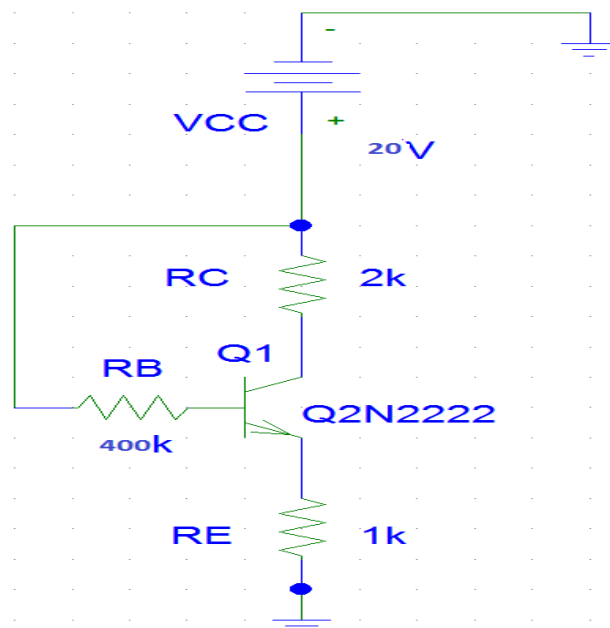
2. Draw the dc load line of the given circuit and calculate the Q-point values of I_C and V_{CE} . Consider $\beta_{dc} = 50$ and $I_C \neq I_E$.



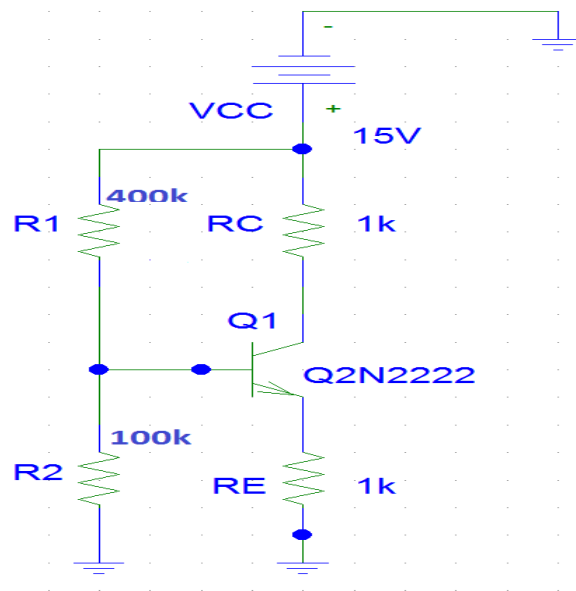
3. Determine I_C and V_{CE} using Thevenin's theorem in the circuit shown below. Assume $\beta_{dc} = 99$ and $I_C \neq I_E$.



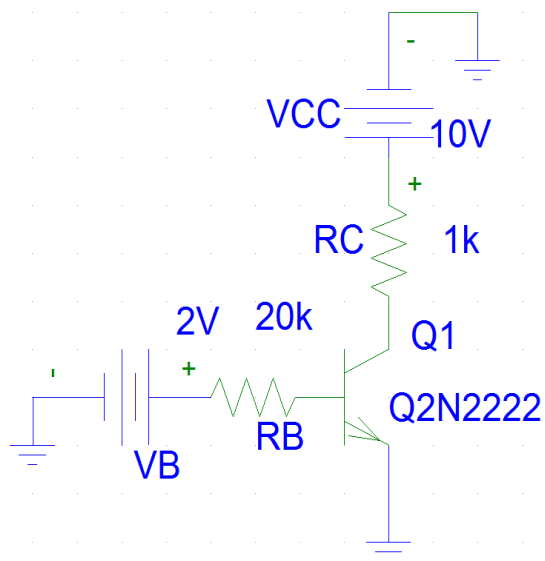
4. Determine the working region of the BJT in circuit below. Assume $\beta_{dc} = 100$.



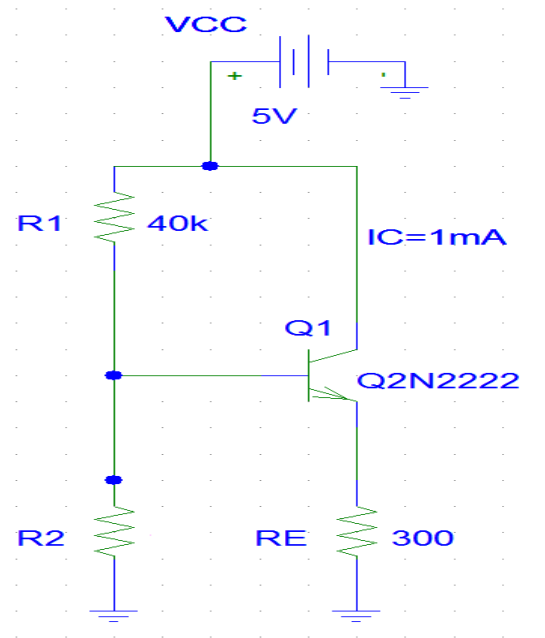
5. Calculate the value of R_2 which results in $I_C = 1mA$ for the Si BJT as shown below. Assume that the BJT has a very high β_{dc} .



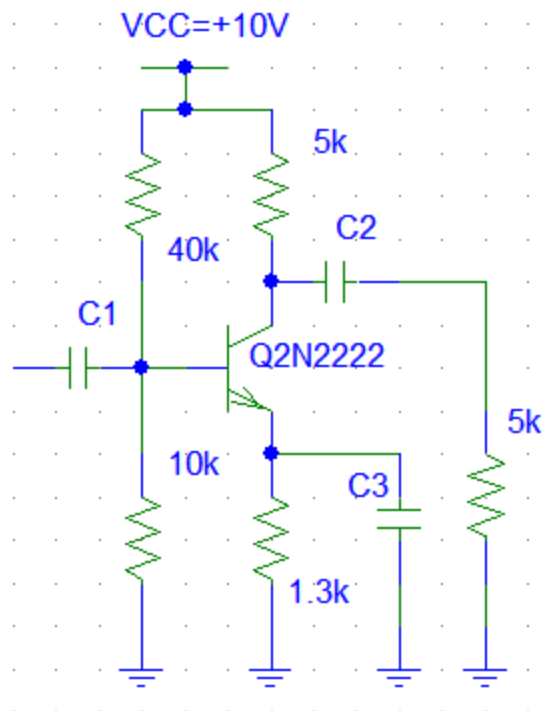
6. For the given circuit, $V_{BE} = 0.7\text{V}$ and β_{dc} is very large. Do the DC analysis and find the value of I_E .



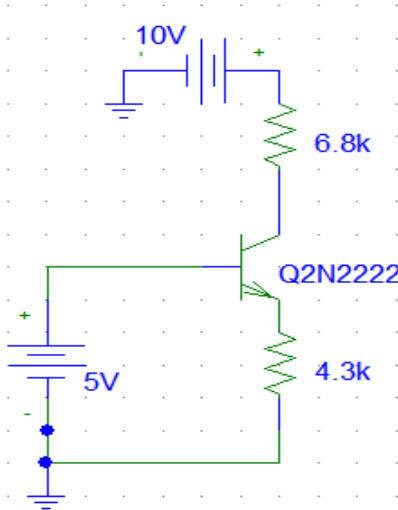7. For problem 6, assume that $V_T=25\text{mV}$ and all the capacitances are very large. Do the small signal analysis and calculate the mid-band voltage gain of the amplifier.
8. Assume, $V_{BE}=0.7\text{V}$ and β_{dc} is very large and identify in which mode the BJT is working.



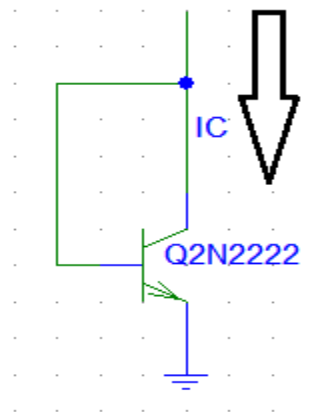9. Assume, $V_{BE}=0.7\text{V}$ and the reverse saturation current of the junction at room temperature is 10^{-14}A . Calculate the emitter current for $\eta=1$.



10. For the circuit shown in below, given that $V_{CE(sat)}=0.2\text{V}$, $\beta_{dc}=200$. Calculate the minimum base current required to drive the BJT in saturation.

