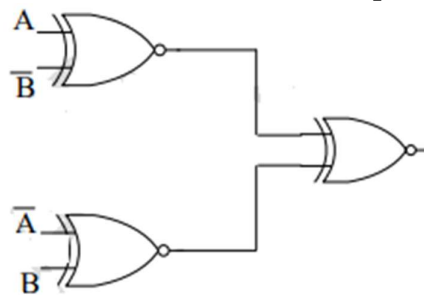


Assignment

- Convert the following BCD number to decimal
 $010101101001_{\text{bcd}}$
- Perform the following operations in 2's complement method (use 8 bit representation)
 - $(52)_{10} - (23)_{10}$
 - $(23)_{10} - (52)_{10}$
 - $(52)_{10} - (-23)_{10}$
- The output of the circuit shown is equal to



- 0
- 1

- $\bar{A}B + A\bar{B}$
- $\overline{(A \oplus B)} \oplus (A \oplus B)$

- The minimized form of the logical expression.
 $(A \bar{B} C + A \bar{B} \bar{C} + A B C + A B \bar{C})$
- Using 4-variable K'Map simplify the Boolean function given by
 $F(w, x, y, z) = \sum m(2, 3, 10, 11, 12, 13, 14, 15)$
- Using K'Map simplify in the product-of-sum form the function given by
 $F(A, B, C, D) = \prod M(0, 6, 10, 12)$
- The Boolean expression for the truth table shown is

CD \ AB	AB			
	00	01	11	10
00	1	1	0	1
01	0	0	0	1
11	1	0	0	0
10	1	0	0	1

8. Use Boolean Algebra to show that

$$A'BC' + AB'C' + AB'C + ABC' + ABC = A + BC'$$

9. Derive the logical expression for sum and carry of a full adder.

10. Implement full adder using half adder.