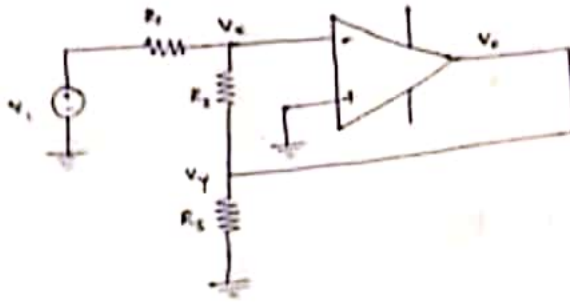


1.



$$V_+ = 0$$

$$V_- = V_+$$


Nodal at x :

$$\frac{V_x - V_1}{R_1} + \frac{V_x - V_0}{R_2} = 0$$


$$\Rightarrow -\frac{V_1}{R_1} - \frac{V_0}{R_2} = 0 \Rightarrow V_0 = -\frac{R_2}{R_1} V_1$$

Voltage gain = $-\frac{R_2}{R_1}$

2.

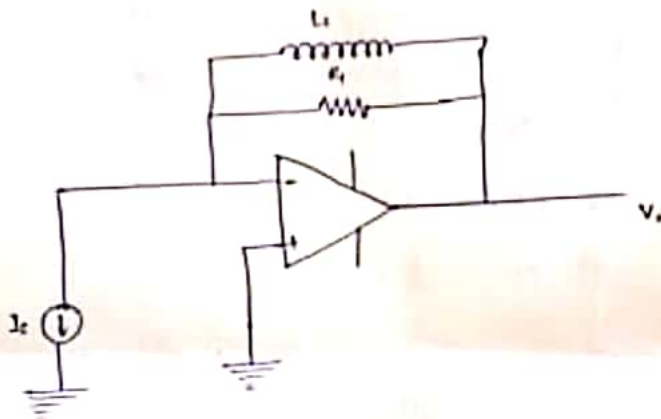


at low frequency:

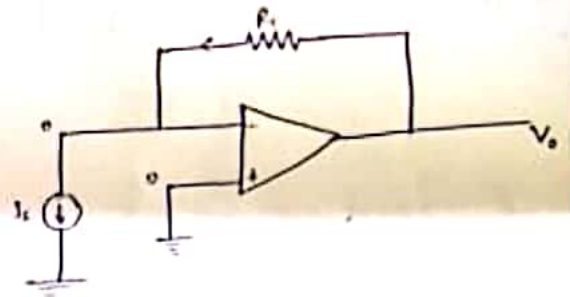


$$V_0 = I_s R_f$$

at high frequency:

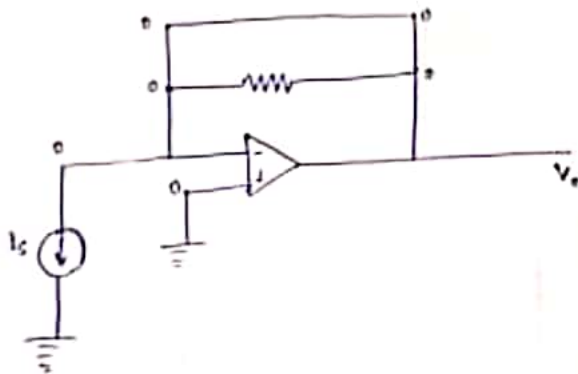

$$V_0 = 0V$$

Hence, low pass filter

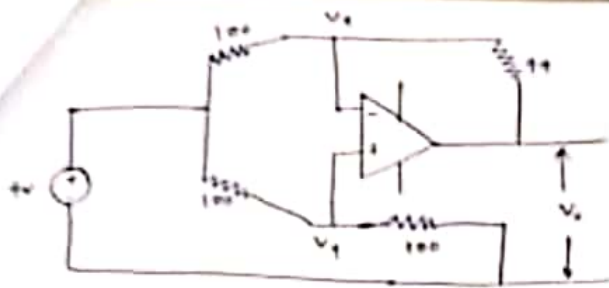

$$V_x = V_y : \quad \frac{4 - V_y}{100} = \frac{V_y}{100} \Rightarrow V_y = 2V$$

$$\frac{4 - 2}{100} = \frac{2 - V_o}{100} \Rightarrow$$

$$V_x = V_y$$


at node x:

$$\frac{4 - V_x}{100} = \frac{V_x - V_o}{100}$$

at node y:

$$\frac{4 - V_y}{100} = \frac{V_y}{100}$$

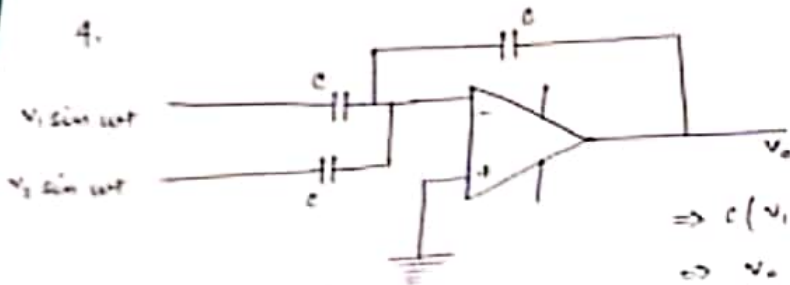
$$V_o = 2 - 100(0.02) = 0.02V \text{ (Ans)}$$



charge of capacitor ① + charge of capacitor ② = charge of capacitor ③

$$\Rightarrow c(V_1 \sin wt) + c(V_2 \sin wt) = c(0 - V_o)$$

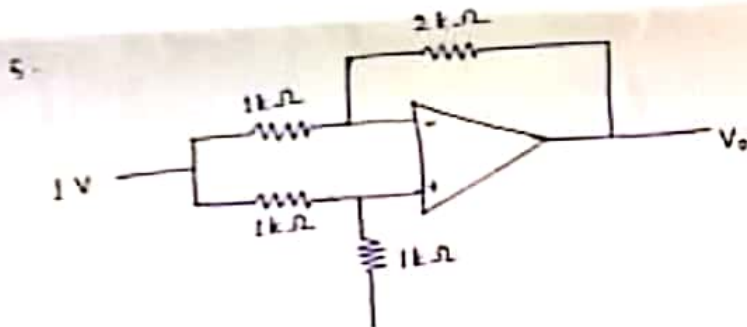
$$\Rightarrow V_o = -(V_1 \sin wt + V_2 \sin wt)$$



$$V_o = -\frac{2(1)}{1} + \left(1 + \frac{2}{1}\right) \times V_i$$

$$\Rightarrow V_o = -2 + 3 \times 1 \times \frac{1}{2}$$
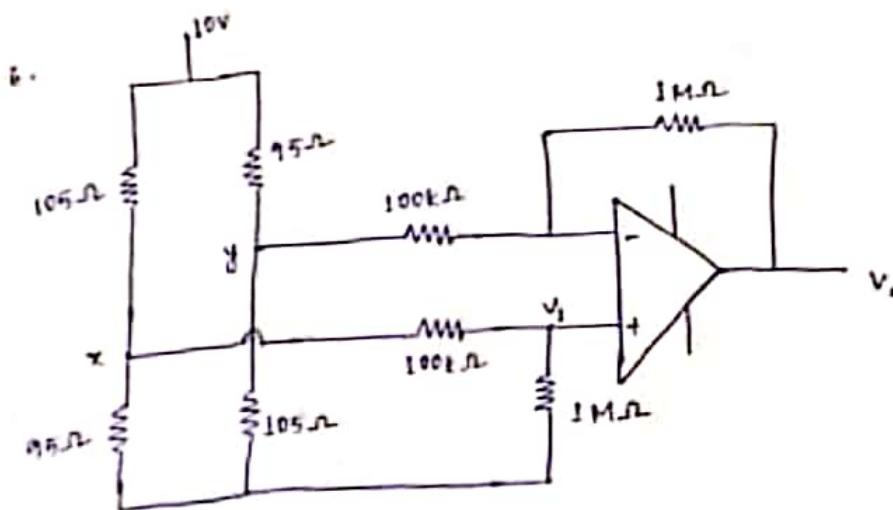
$$= -2 + 1.5 \Rightarrow \boxed{V_o = -0.5V}$$



$$V_i = \frac{x \times 10^5}{10^5 + 100} = 0.9x$$

$$\Rightarrow x = 1.1V_i$$

Applying nodal at x

$$\frac{x-10}{105} + \frac{x}{95} + \frac{x-V_1}{100} = 0$$

$$\Rightarrow \frac{1-1V_1-10}{105} + \frac{1-1V_1}{95} + \frac{1-1V_1-V_1}{100} = 0$$

$$\Rightarrow V_1 \left[\frac{1.1}{105} + \frac{1.1}{95} + \frac{0.1}{100} \right] = \frac{10}{105} \Rightarrow \boxed{V_1 = 4.13V}$$

Applying nodal at y:

$$\frac{y-10}{95} + \frac{y}{105} + \frac{y-V_1}{100} = 0$$


$$\Rightarrow \frac{y-10}{95} + \frac{y}{105} + \frac{y-4.13}{100} = 0$$

$$\Rightarrow y = \frac{10}{95} + \frac{4.13}{100} = \boxed{4.87V}$$



$$\left(\frac{1}{95} + \frac{1}{105} + \frac{1}{100} \right)$$

$$V_o = -\frac{10^3}{100} \times 4.87 + \left(1 + \frac{10^3}{100} \right) \times 4.13$$
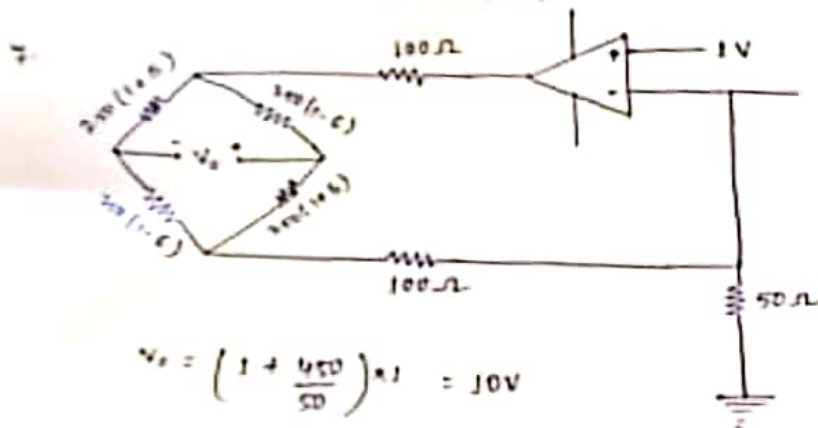
$$V_o = \underline{\underline{-3.27V \text{ (Ans)}}}$$


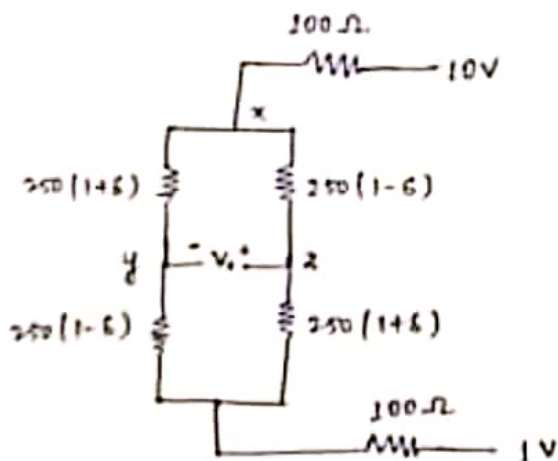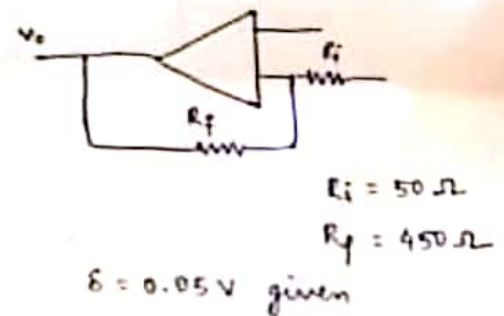
$$V_o = \left(1 + \frac{450}{50} \right) \times 1 = 10V$$



$$i = \frac{9}{450} = 0.02A$$

$$V_1 = 10 - 100 \times 0.02 - 0.01 \times 250(1+\delta)$$

$$= 5.5 - 0.01\delta$$

$$V_2 = 10 - 100 \times 0.02 - 0.01 \times 250(1-\delta)$$


$$= 5.5 + 0.01\delta$$

$$\Rightarrow V_o = V_2 - V_1$$

$$= 0.02\delta$$

$$= 0.02 \times 0.05$$

$$= 0.0010V$$

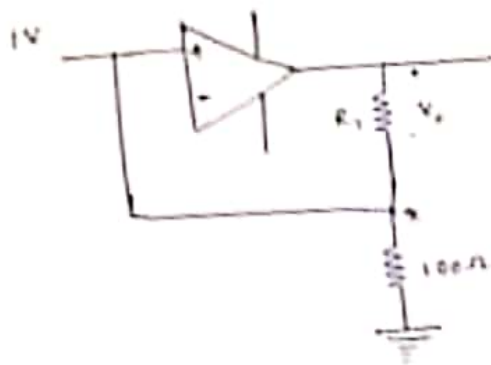

since op-amp is ideal


$$V_+ = 1V$$

applying KVL in loop (I)

$$-V_x - V_x = 0$$

$$\Rightarrow V_x = -V_x$$

$$\Rightarrow \boxed{V_x = -1V}$$

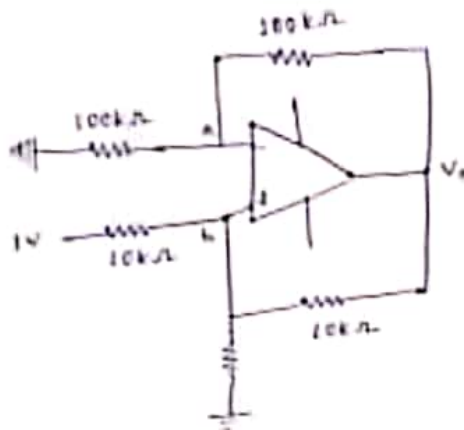

Applying nodal at b:


$$\frac{V_x - 1}{10} + \frac{V_x}{R_L} + \frac{V_x - V_x}{10} = 0$$

$$\Rightarrow \left(\frac{V_x}{10} + \frac{V_x - V_x}{10} \right) - \frac{1}{10} + \frac{V_x}{R_L} = 0$$

$$\Rightarrow 0 - \frac{1}{10} + \frac{V_x}{R_L} = 0$$

$$\boxed{\frac{V_x}{R_L} = I_L} \Rightarrow I_L = 0.1mA \Rightarrow \boxed{I_L = 100\mu A}$$

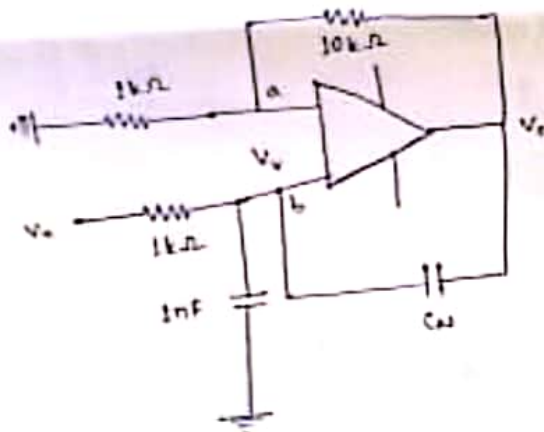Applying nodal at a: $\frac{V_x}{100} + \frac{V_x - V_x}{100} = 0 \Rightarrow \frac{V_x}{10} + \frac{V_x - V_x}{10} = 0$



Applying nodal at A:

$$\frac{V_x}{1} + \frac{V_x - V_x}{10} = 0$$

$$\Rightarrow V_x = (1+10)V_x = 11V_x$$

Applying Nodal at b:

$$(V_x - V_x) \times 10^{-3} = 10^{-9} \frac{d(V_x)}{dt} + \frac{d(V_x - V_x)}{dt} C_x$$

$$= 10^{-9} \frac{d}{dt} V_x - \frac{d}{dt} 10V_x C_x$$

$$(V_x - V_x) \times 10^{-3} = (10^{-9} - 10C_x) \frac{d}{dt} V_x$$

Given $V_x = V_x$

$$10^{-9} - 10C_x = 0$$

$$C_x = 10^{-10} F$$

$$\therefore 1pF = 10^{-12} F$$

$$\boxed{C_x = 100pF}$$