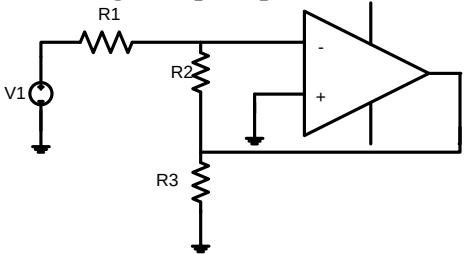
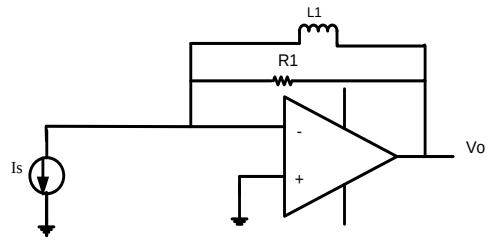
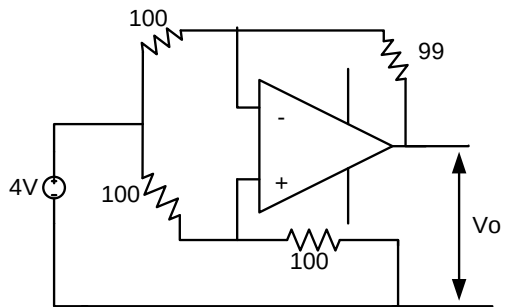
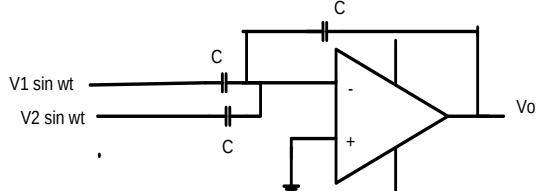
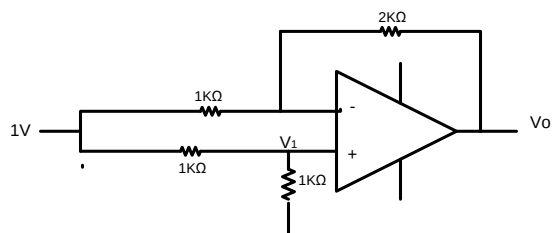
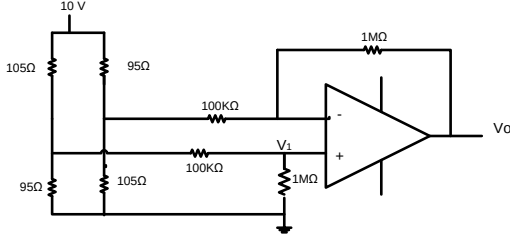
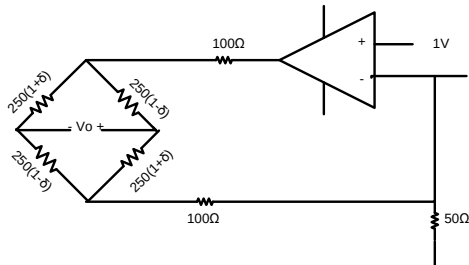
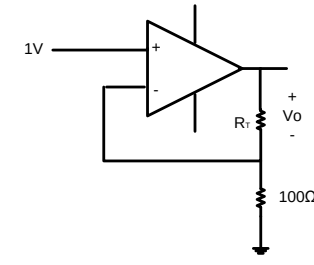
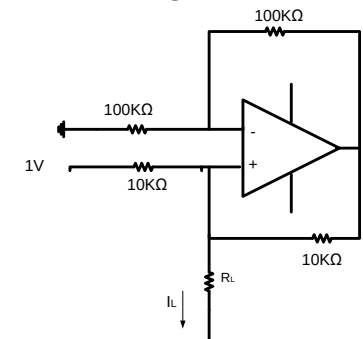


OP-AMP ASSIGNMENT QUESTIONS

Q.1	Assuming the op-amp to be ideal, the voltage gain of the amplifier shown below is _____. 
Q.2	The circuit below implement a filter between the input current I_s and output voltage V_o, the op-amp is ideal. The filter implemented is a _____. a) High Pass b) low pass c) band pass d) band reject 
Q.3	For the ideal Op-Amp circuit of figure. Determine the output voltage V_o _____. 
Q.4	If the op-amp in the figure, is ideal then V_o is _____. 
Q.5	For the Op-Amp circuit shown in the figure. V_o is _____. 

Q.6	For the Op-Amp circuit shown below, V_0 is approximately equal to ____. 
Q.7	In the circuit shown, assume that the Op-Amp is ideal. The bridge output voltage V_0 (in mV) for $\delta=0.05$ is ____. 
Q.8	In the figure shown, R_T represents a resistance temperature device (RTD), whose characteristic is given by $R_T = R_0(1 + \alpha T)$, where $R_0 = 100\Omega$, $\alpha = 0.0039^\circ/\text{C}$ and T denotes the temperature in $^\circ\text{C}$. Assuming the op-amp to be ideal, the value of V_0 in volts when $T = 100^\circ\text{C}$ is ____ V. 
Q.9	In the circuit given below, the OP-AMP is ideal. The value of current I_L in microampere is ____ 
Q.10	In the circuit given below, the OP-AMP is ideal. The input V_X is a sinusoid. To ensure $V_X = V_V$ the value of C_N in picofarad is ____ 