


ELECTRONICS ENGINEERING DEPARTMENT IIT (ISM) DHANBAD
SEMESTER MONSSON 2018-1019

EXAMINATION: END SEMESTER EXAMINATION
SEMESTER B.TECH. 1ST SEMESTER (GROUP E, F, G, H)
SUBJECT: ECC 11101 ELECTRONIC ENGINEERING

TIME: 3 HRS
MAX MARKS: 100

INSTRUCTIONS: ANSWER ALL QUESTIONS FROM PART I, AND ANY TWO QUESTIONS FROM PART II.
MAKE SUITABLE ASSUMPTIONS WHEREVER NECESSARY

PART I



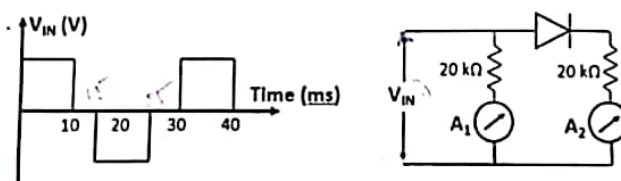
Q.1	State whether the following statements are TRUE or FALSE (T/F). Give appropriate reasoning (R) for your answer in brief. a. An ideal op amp has voltage gain of the order of 10^6 A/A. b. Waveforms can be shaped easily by using a combination of diode, capacitor and battery. c. A rectifier converts alternating current into a unidirectional current. In a half-wave rectification with input voltage $V_m \sin \omega t$ and a resistive load R_L , the dc current $I_{dc} = V_m / \pi R_L$. d. In a digital circuit we have the output given as $\overline{(\overline{A} + \overline{B})} + \overline{C}$. This expression is equivalent to $BC + AC$. e. The number $(5F)_{16}$ is equivalent to $(96)_{10}$.	$5 \times (1(T/F) + 3(R))$ = 20 Marks
Q.2 (a)	The signal V_{IN} is applied to the circuit shown in Figure 1. Predict the reading on the two meters A_1 and A_2 , if they are DC ammeters.  Figure 1	10 marks
Q.2 (b)	A four-variable logic function comprises of following max-terms: $\prod M(3,7,9,13,15)$. Deduce the minimized SOP form using k-map. Draw the corresponding logic circuit. $(A+B)(A+C)(A+D)$	10 marks
Q3 (a)	A Silicon semiconductor doped with 10^{17} cm^{-3} phosphorus atoms has been used to design a humidity sensor. In May 2018, the sensor was tested at Delhi, India (35°C); Aziziyah, Libya (50°C); Melbourne, Australia (14°C) and Talvik, Norway (-5°C). Numbers inside the parenthesis represent the temperature of the place. When an electric field of 1 MV/m was applied, 16 kA/cm^2 current density was observed in the Silicon sensor. Assuming the diffusivity to be independent of temperature, in which place/city the measurement was performed? Electron mobility $0.135 \text{ m}^2/\text{V.s}$, Hole mobility $0.048 \text{ m}^2/\text{V.s}$	10 marks




$$D_n = 218 \text{ cm}^2/\text{s}, D_p = 1 \text{ cm}^2/\text{s}$$

$$16 \times 10^3 \text{ A/cm}^2 = e n D_n \frac{dV}{dx} + e p D_p \frac{dV}{dx}$$

Scanned by CamScanner

Scanned by CamScanner

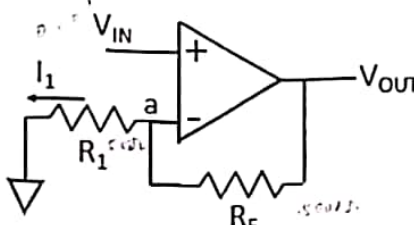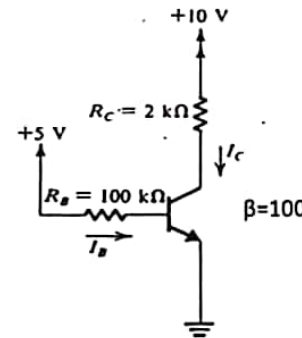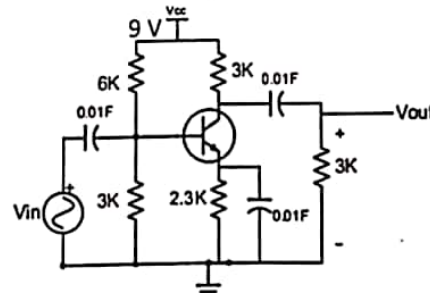Q. 3 (b)	An ideal op-amp amplifier is shown in Figure 2, where $R_1 = 5 \text{ k}\Omega$ and $R_F = 500 \text{ k}\Omega$. Evaluate the voltage gain V_{OUT}/V_{IN}. For an input voltage $V_{IN} = 0.01 \text{ V}$, what is V_a and I_1?  Figure 2	10 marks
Q.4 (a)	For the circuit shown in Figure 3, determine the currents I_B, I_C, I_E and V_{CE}. Assume $V_{BE} = 0.7 \text{ V}$, $V_T = 25 \text{ mV}$.  Figure 3	10 marks
Q. 4 (b)	A CE amplifier circuit is shown in Figure 4. Assume $V_{BE} = 0.7 \text{ V}$, $V_T = 25 \text{ mV}$. - Find the DC collector current (I_C) and the collector to emitter voltage (V_{CE}). - Draw the small signal equivalent circuit. - Evaluate the mid-band voltage gain $\frac{V_{OUT}}{V_{IN}}$.  Figure 4	10 marks

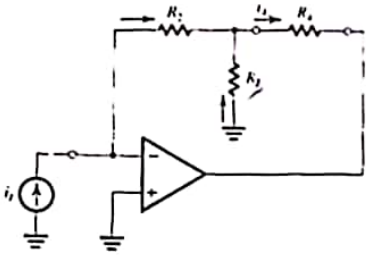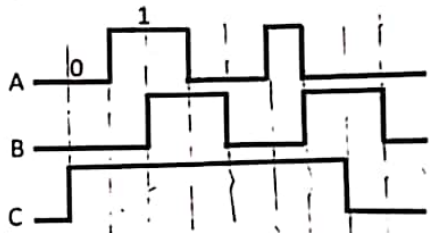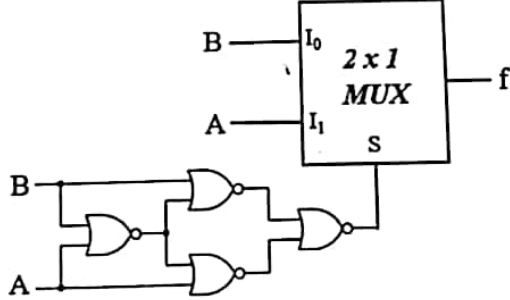Q5 (a)	Design an op-amp adder circuit to give an input-output relationship of: $V_{out} = 4V_1 + 5V_2$, where V_1 and V_2 are voltages applied toward the inverting and non-inverting terminal respectively. Assume the value of feedback resistor as 100 k Ω .	10 marks
Q. 5 (b)	For the circuit shown in Figure 5, show that $i_4 = i_1 (1 + \frac{R_2}{R_3})$. Assume the op amp to be ideal.	10 marks
 Figure 5		
Q6 (a)	Using the following waveforms shown in Figure 6, draw the waveform of X, where $X = AC + B'$.	10 marks
 Figure 6		
Q6 (b)	Using the above wavefunctions A and B, draw the waveform of f for the logic circuit in Figure 7..	10 marks
 Figure 7		